

Quadrature Down Converter

KEERTHI SEELA

2023102012

IIT Hyderabad

keerthi.seela@students.iit.ac.in

ANUMULA VENKATA SAI SREE SAHITHI

2023112002

IIT Hyderabad

sahithi.anumula@research.iit.ac.in

Abstract—The objective of this project is to develop a Quadrature Down Converter (QDC), enabling frequency down-conversion. The project will involve a comprehensive analysis of system requirements, followed by the design, simulation, and practical realization of the QDC. Through systematic examination of operational needs, circuit design, virtual testing, and physical implementation.

Keywords—Quadrature Oscillator, Mixer circuit, low pass filter

I. INTRODUCTION (HEADING 1)

The quadrature down converter converts the high-frequency quadrature signals into low-frequency signals. This conversion is essential for extraction of information from received signals. Internally, a quadrature down converter preserves the in-phase (I) and quadrature-phase (Q) components of the input signal while shifting its frequency. This is typically achieved through a combination of mixing, filtering, and amplification stages integrated into the converter's design.

In this project, we are developing a quadrature down converter by choosing and integrating essential components like mixers, filters, and oscillators. The primary goal is to create a high-performance system that can effectively convert high-frequency signals to low-frequency signals while preserving signal integrity. This involves optimizing each stage of the down converter to achieve efficient frequency conversion.

A QDC has three main components. They are:

1) Quadrature Oscillator:

This oscillator circuit generates two high-frequency signals characterized by a phase disparity of 90° .

2) Mixer Circuit (or) Switch:

This circuit (which includes MOSFET as an important component) performs signal mixing by combining two input signals, one sourced externally and the other derived from the oscillator, resulting in the generation of a mixed signal.

3) Low Pass Filter:

This filter selectively attenuates high-frequency signals while allowing low-frequency signals to pass through, based on its defined cut-off frequency.

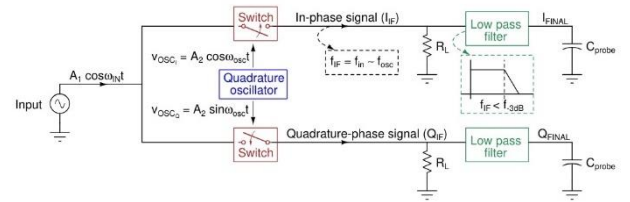


Fig.1: Quadrature Down Converter

II. CIRCUIT ANALYSIS

The Quadrature Oscillator is given an input of 0V, so the offset DC voltage is taken as input and the op-amp amplifies it to sine wave and cosine waves. Op Amps are used to give a negative feed-back and add a phase of 180° in each feedback. If a phase difference of 90° is given as feed-back then, the amplitude would continuously rise. To avoid this, we need to make it 180° . In a Quadrature Down-Conversion (QDC) oscillator, the integrator and phase shifter are crucial components that work together to generate quadrature (90° -degree phase-shifted) signals. These signals are essential in various applications, including frequency synthesis, modulation, and demodulation.

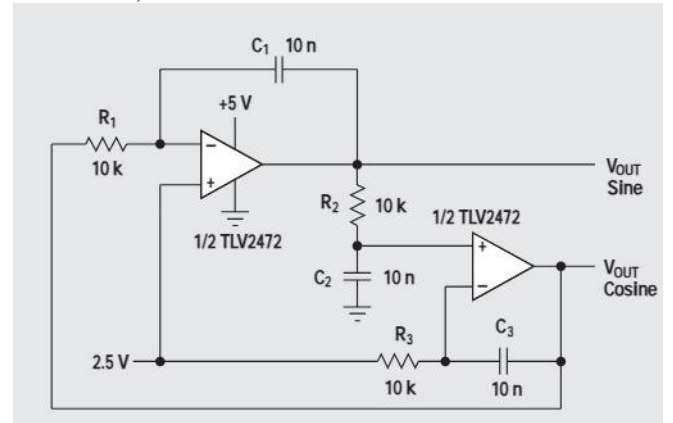


Fig.2: Quadrature Oscillator

The mixer circuit (switch) contains a MOSFET which operates in Triode region and the following is the working of it.

The working of the circuit is as follows:

- Voltage input from the oscilloscope = $V_{OSC} = A_1 \sin(2\pi t - 100k)$
- Voltage input from the external source =

$$V_{IN} = A_2 \sin(2\pi t - 99k)$$

• Biasing Voltage = V_{BIAS}

$$V_g = V_{BIAS} + V_{OSC}$$

$$V_s = V_{IN}$$

$$V_b = 0$$

Now,

$$V_{GS} = V_{BIAS} + V_{OSC} + V_{IN}$$

V_{bias} is approximated to the value of Threshold voltage of MOSFET

$$\therefore V_{GS} - V_{TH} = V_{OSC} - V_{IN}$$

$$\therefore \text{if } V_{OSC} - V_{IN} < 0$$

$$\Rightarrow I_{DS} = 0$$

\Rightarrow the MOSFET is in Cut-off Region.

if

$$V_{OSC} - V_{IN} > 0$$

\Rightarrow the MOSFET is in Triode region

Note that the MOSFET never goes to saturation, because:

$$V_{OUT} \ll V_{IN} \ll V_{OSC}$$

$$V_{DS} - V_{GS} = V_{OUT} - V_{IN} - V_{BIAS} - V_{OSC} + V_{IN}$$

$$V_{DS} - V_{GS} = V_{OUT} - V_{BIAS} - V_{OSC}$$

$$V_{DS} - V_{GS} < -V_{BIAS}$$

for a triode to be in saturation,

$$V_{DS} > V_{GS} - V_{TH}$$

But, this condition is never satisfied. So, it can be said that MOSFET never enters saturation

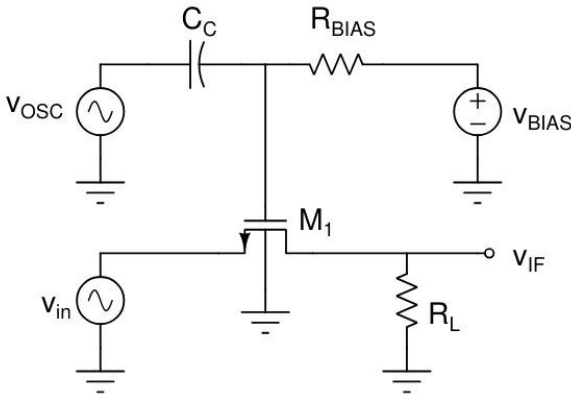


Fig.3: Mixer

A low-pass filter is designed to reduce or suppress high-frequency signals while allowing low-frequency signals to pass through with minimal alteration. The cutoff frequency marks the point where the filter begins attenuating higher frequencies. The roll-off characteristic indicates how rapidly the filter's attenuation increases beyond this cutoff frequency

$$F_c = 1/2\pi RC$$

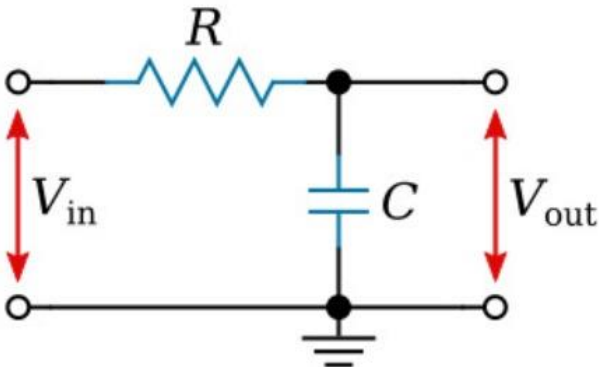


Fig.4: Low pass filter

III. QUADRATURE OSCILLATOR DESIGN

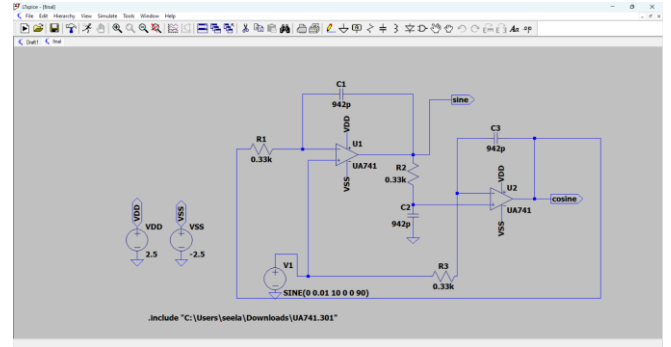


Fig.5: LTSPICE of Quadrature Oscillator

2. Given freq of V_{osc1} & $V_{osc2} = 100kHz$

$$f = \frac{1}{2\pi RC}$$

$$RC = \frac{1}{2\pi f}$$

$$RC = \frac{1}{200k\pi}$$

$$RC = 1.59 \times 10^{-6}$$

Ideally we have to take

$$RC = 1.59 \times 10^{-6}$$

But for the equipment needs,

we have took

$$R = 0.3k$$

$$C = 942p$$

Fig.6: Calculations of R and C

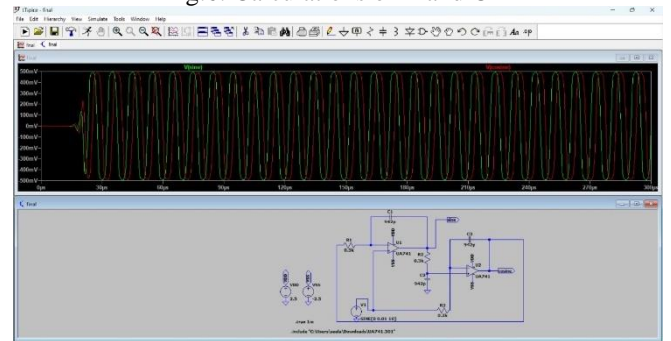


Fig.7: V_{osc1} and V_{osc2} Transient Plots

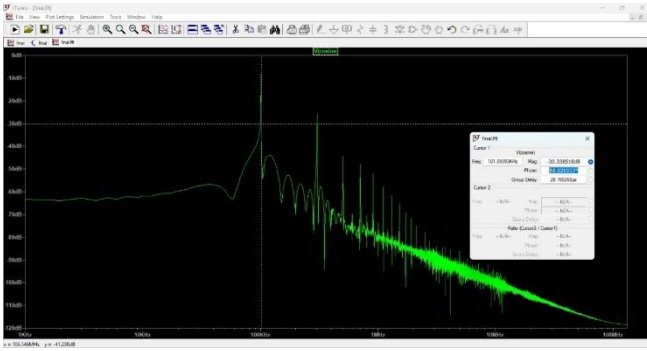


Fig.8: FFT of cosine

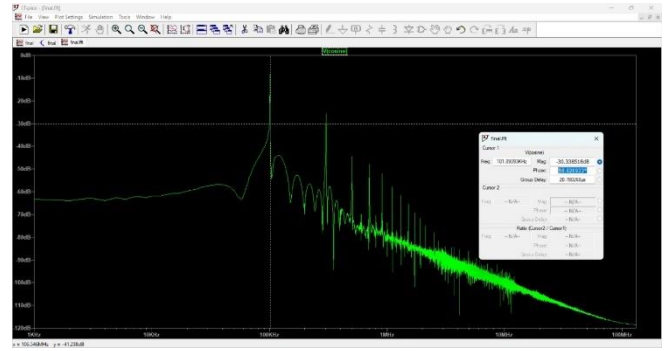


Fig.11: Phase of cosine

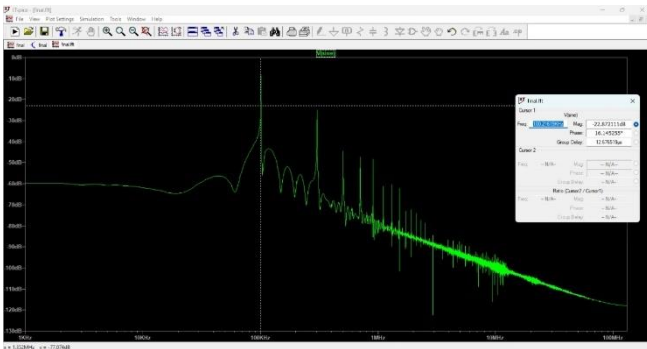


Fig.9: FFT of sine

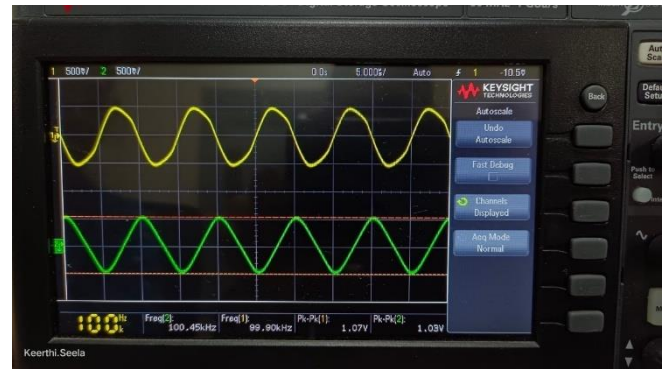


Fig.12: Transient waveforms

To calculate phase diff

$$\phi_1 - \phi_2 = 2\pi f (t_{\text{peak sine}} - t_{\text{peak cosine}})$$

$$= 360 \times 100k \times (2.498 \mu s)$$

$(t_{\text{peak sine}} - t_{\text{peak cosine}})$ is obtained

from transient simulations in Ltspice.

$$= 36 \times 2.498$$

$$= 89.928^\circ$$

$$\approx 90^\circ$$



Fig.13: FFT of sine



Fig.14: FFT of cosine

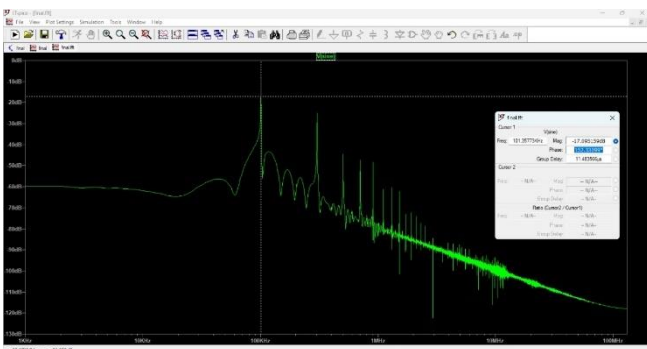


Fig.10: Phase of sine



Fig.15: Phase difference

IV. SWITCH(MIXER) DESIGN

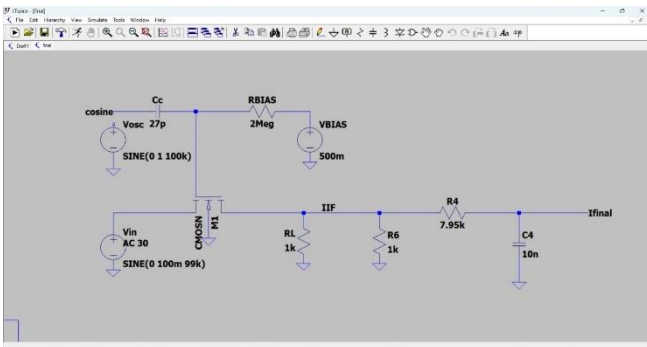


Fig.16: LTSPICE of Mixer

$$V_{IF1} = V_{in} \times V_{osc} = \frac{A_1 A_2}{2} \left[\cos(\omega t) \right]$$

In the given circuit

$$V_{in} = 100 \text{ mV} \quad V_{gsc} = 1 \text{ V}$$

$$\frac{A_1 A_2}{2} = \frac{1 \times 100 \text{ mV}}{2} = 50 \text{ mV}$$

V_{IF1} 's Amplitude calculated through LT spice

$$= 48 \text{ mV} \approx 50 \text{ mV}$$

So, when the V_{osc} 's sine wave is in Positive values the circuit system operates in On Condition, if it is in negative values, system circuit operates in off Condition.

As $V_{osc} > V_T$ of MOSFET \rightarrow on Condition

Fig.17: Working of mixer

$$f = \frac{1}{2\pi RC}$$

$$V_{bias} = V_{th} \text{ of MOSFET}$$

to allow 100kHz in to the circuit

$$100 \text{ kHz} > \frac{1}{2\pi RC}$$

$$RC > \frac{1}{2\pi \times 10^5}$$

$$RC > \frac{10^{-5}}{2\pi}$$

we choose R_{bias} as $2 \text{ M}\Omega$

C_c as 27 pF

Because C_c should be small enough

to allow V_{osc} , whereas R_{bias}

should be high enough, so that

V_{osc} Completely enters into MOSFET

MOSFET parameters

$$2. \frac{W}{L} = \frac{1.8 \mu}{0.18 \mu}$$

$$V_{DS} = 50 \text{ mV}$$

$$V_{BS} = 0 \text{ V}$$

a) From LTspice simulations, we got maximum

$$\text{slope } m = 161.0858 \mu\Omega^{-1}$$

$$\text{at } (x, y) = (716.57183 \text{ mV}, 26.465053 \mu\text{A})$$

$$y - 26.465053 \mu\text{A} = (161.0858 \mu\Omega^{-1})(x - 716.57183 \text{ mV})$$

(y=0) For x-intercept,

$$\frac{-26.465053 \mu\text{A}}{161.0858 \mu\Omega^{-1}} + 716.57183 \text{ mV} = x$$

$$V_{T0} = 0.55228017 \text{ V}$$

Calculation of $V_T = V_{BIAS}$

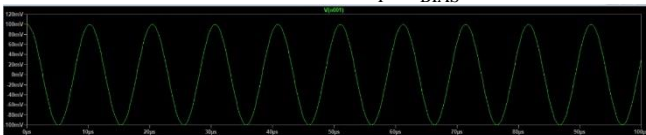


Fig.18: Transient plot of V_{in}

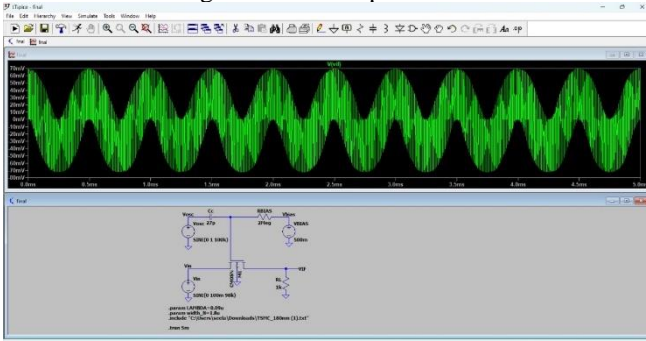


Fig.19: Transient plot of V_{IF} for $f=98\text{kHz}$

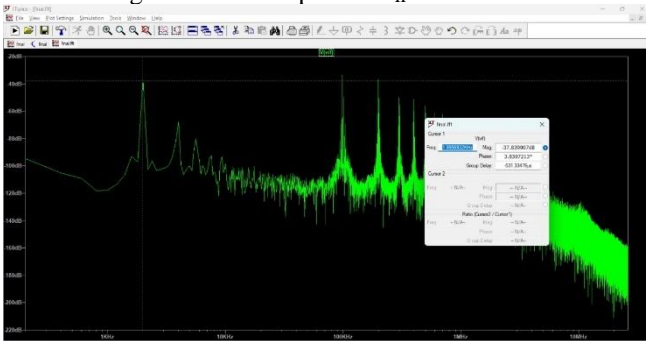


Fig.20: FFT of V_{IF} for $f=98\text{kHz}$

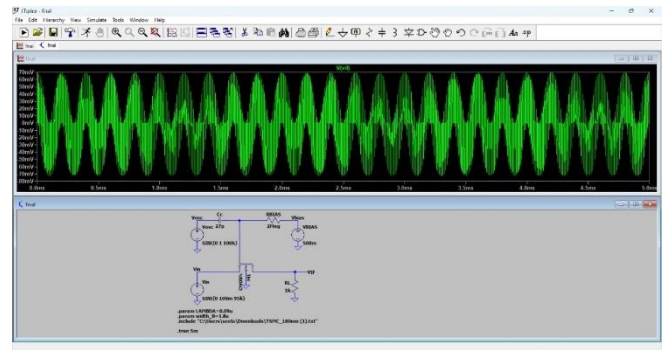


Fig.21: Transient plot of V_{IF} for $f=95\text{kHz}$

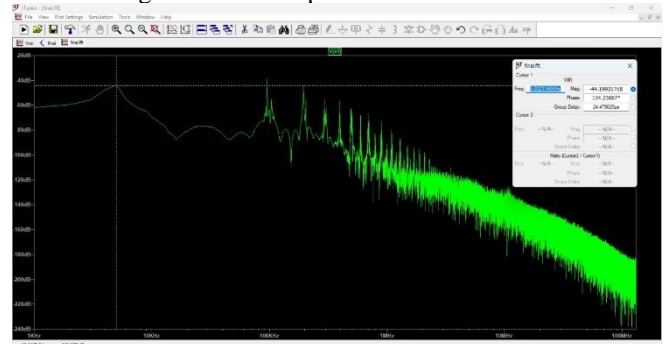


Fig.22: FFT of V_{IF} for $f=95\text{kHz}$

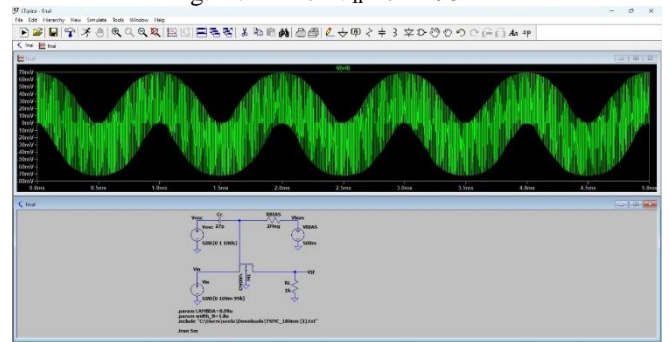


Fig.23: Transient plot of V_{IF} for $f=99\text{kHz}$

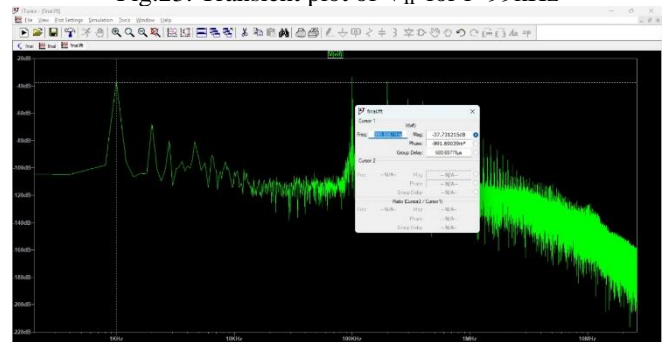


Fig.24: FFT of V_{IF} for $f=99\text{kHz}$

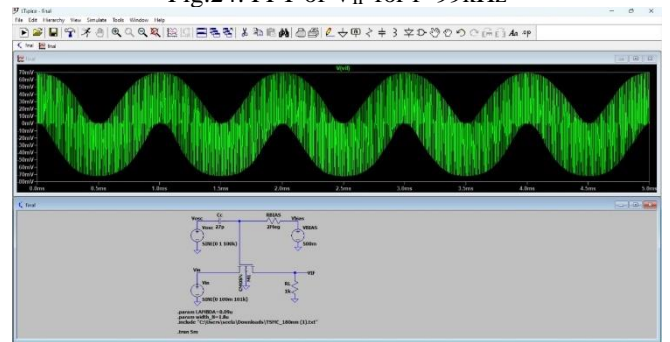


Fig.25: Transient plot of V_{IF} for $f=101\text{kHz}$

HARDWARE OF MIXER CIRCUIT

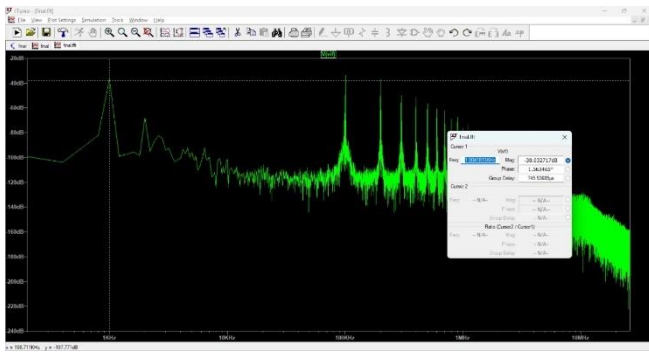


Fig.26: FFT of V_{IF} for $f=101\text{kHz}$

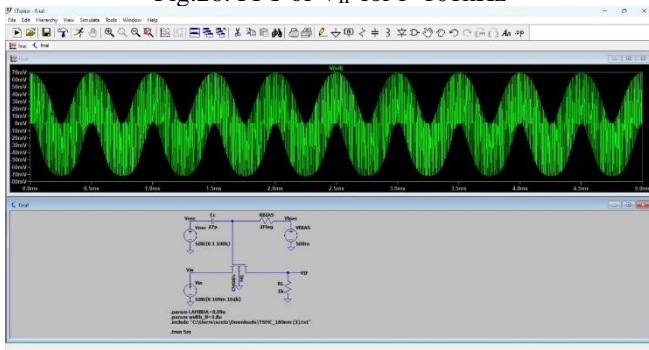


Fig.27: Transient plot of V_{IF} for $f=102\text{kHz}$

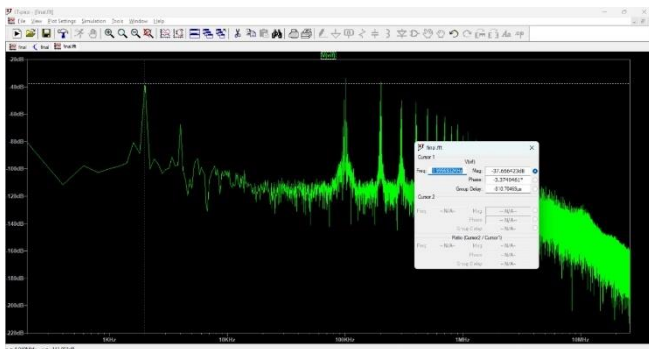


Fig.28: FFT of V_{IF} for $f=102\text{kHz}$

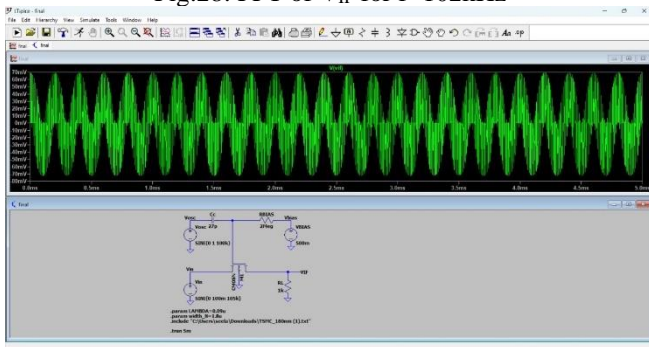


Fig.29: Transient plot of V_{IF} for $f=105\text{kHz}$

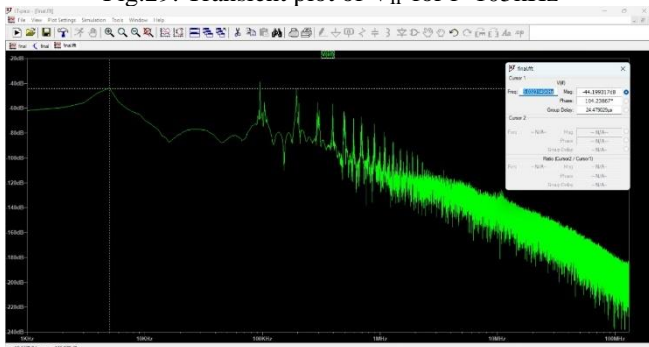


Fig.30: FFT of V_{IF} for $f=105\text{kHz}$



Fig.31: Transient plot of V_{IF} for $f=95\text{kHz}$



Fig.32: FFT of V_{IF} for $f=95\text{kHz}$

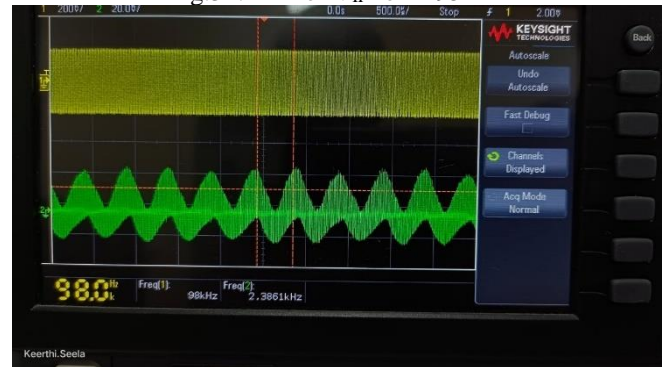


Fig.33: Transient plot of V_{IF} for $f=98\text{kHz}$

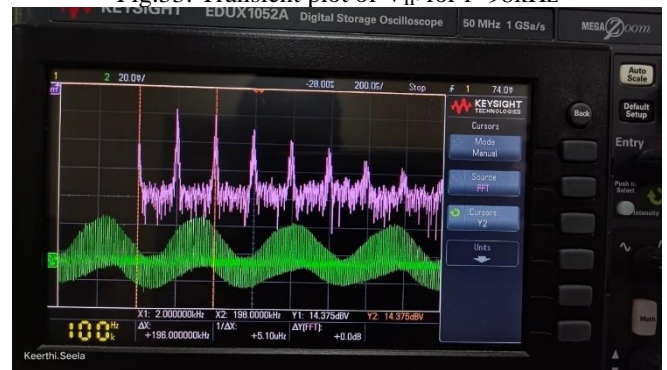


Fig.34: FFT of V_{IF} for $f=98\text{kHz}$

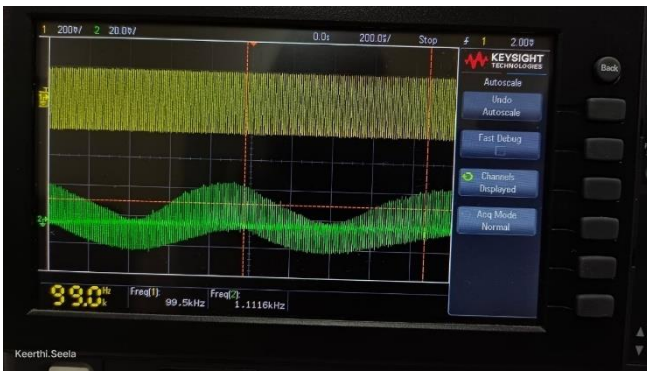


Fig.35: Transient plot of V_{IF} for $f=99\text{kHz}$



Fig.39: Transient plot of V_{IF} for $f=102\text{kHz}$

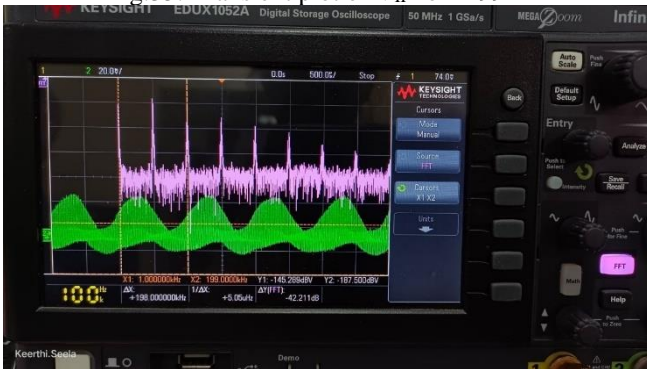


Fig.36: FFT of V_{IF} for $f=99\text{kHz}$



Fig.40: FFT of V_{IF} for $f=102\text{kHz}$



Fig.37: Transient plot of V_{IF} for $f=101\text{kHz}$

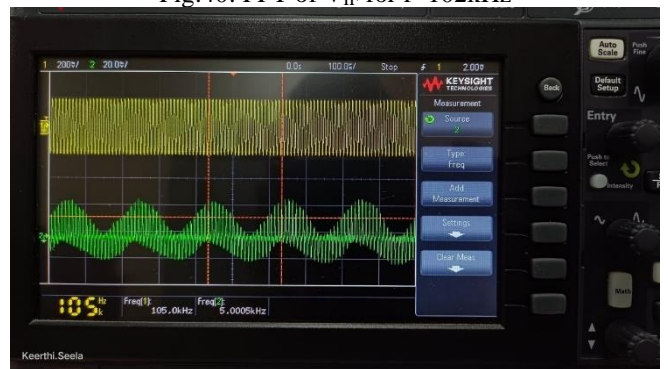


Fig.41: Transient plot of V_{IF} for $f=105\text{kHz}$

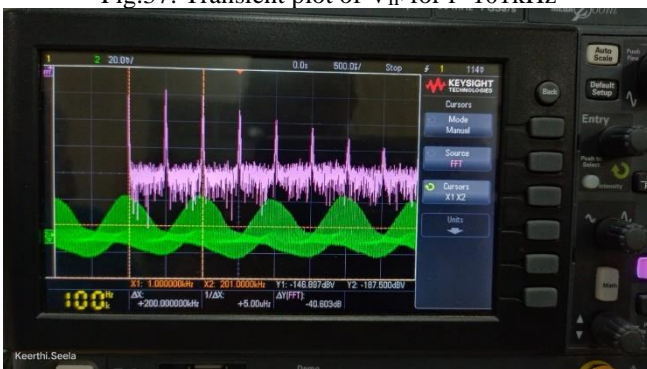


Fig.38: FFT of V_{IF} for $f=101\text{kHz}$



Fig.42: FFT of V_{IF} for $f=105\text{kHz}$

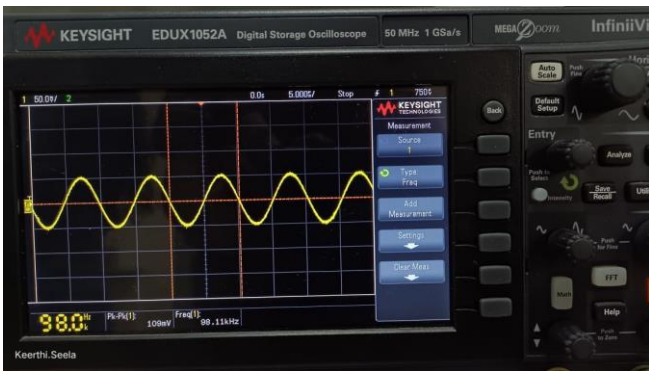


Fig.43: Transient plot of V_{IN}

V. LOW PASS FILTER DESIGN

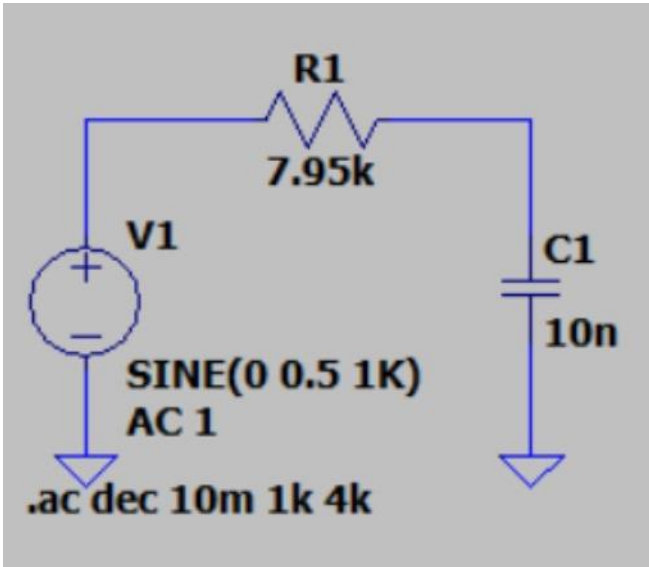


Fig.44: Design of LPF

$$-3\text{dB at } 2\text{kHz}$$

$$\frac{1}{2\pi RC} = 2\text{kHz}$$

$$RC = 7.95 \times 10^{-5}$$

$$R = 7.95\text{K} \approx 8\text{k}\Omega$$

$$C = 10\text{nF}$$

Fig.45: Calculations of R and C

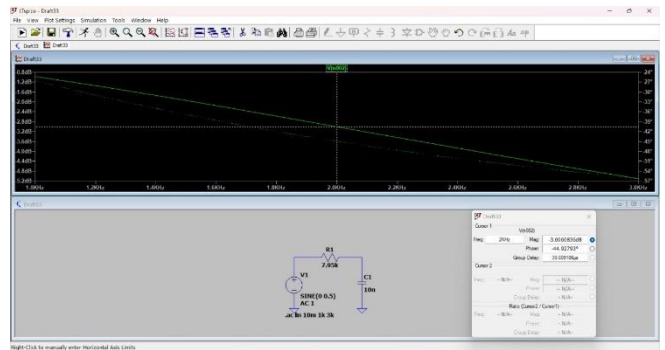


Fig.46: Frequency response

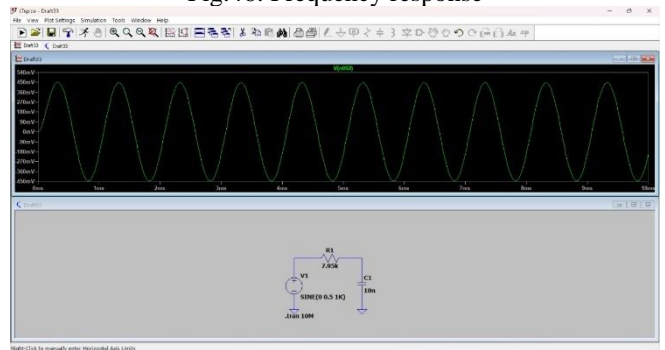


Fig.47: Transient response for 1kHz

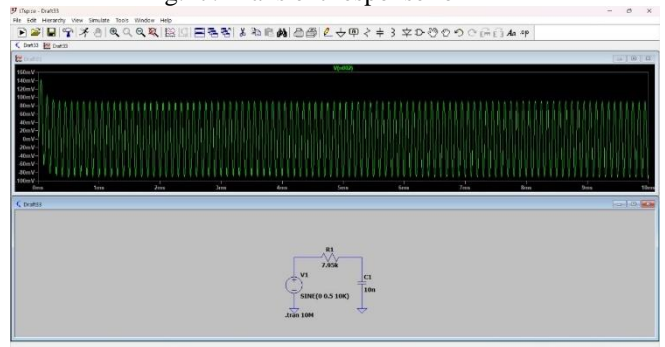


Fig.48: Transient response for 10kHz



Fig.49: LPF FFT

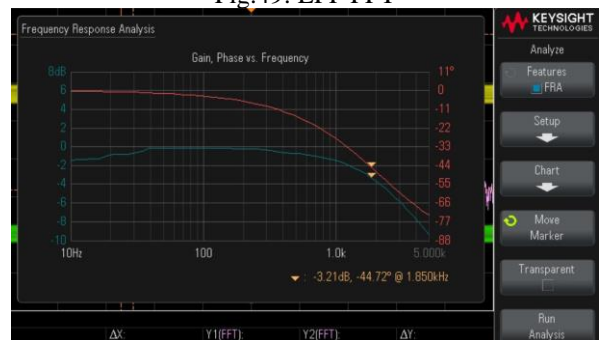


Fig.50: Frequency response in Hardware

VI. COMPLETE CIRCUIT PROTOTYPE DESIGN

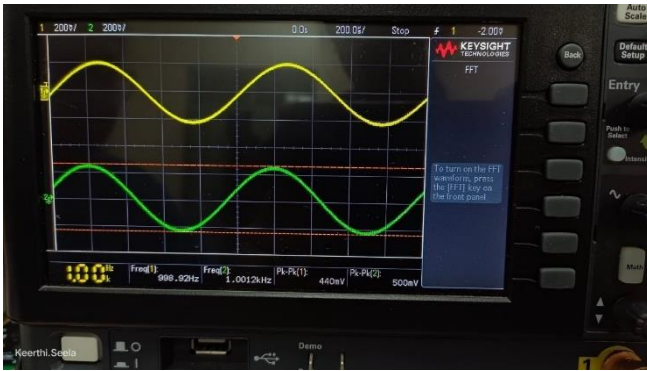


Fig.51: Transient response for 1kHz

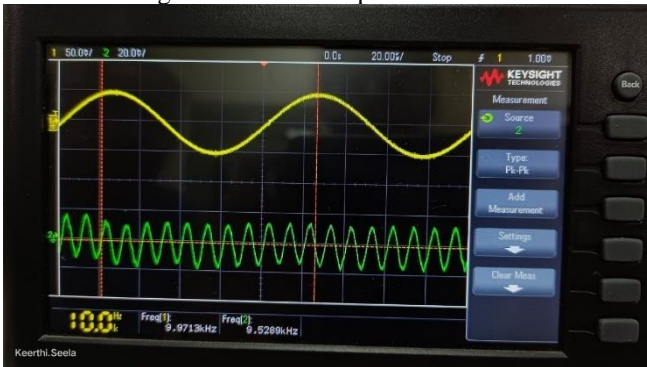


Fig.51: Transient response for 10kHz

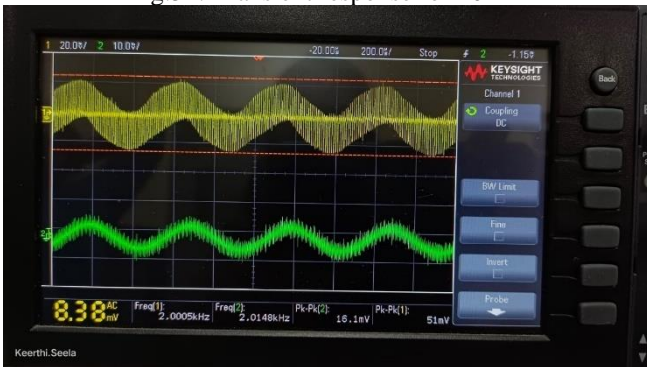


Fig.52: Outputs of Mixer and LPF when connected



Fig.53: FFT of LPF output
When Mixer and LPF are connected

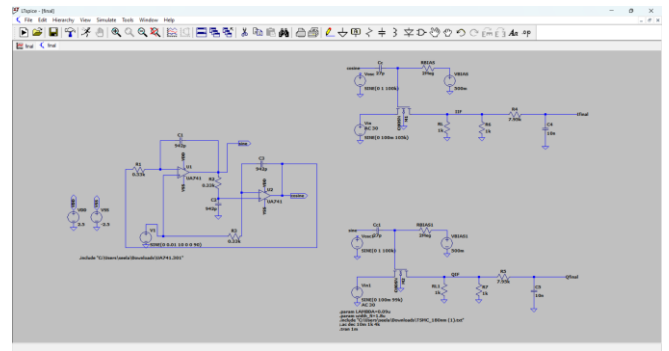


Fig.54: Complete Circuit LTSPICE

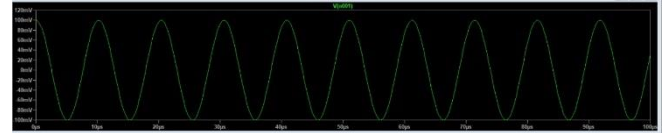


Fig.55: Transient simulation of input

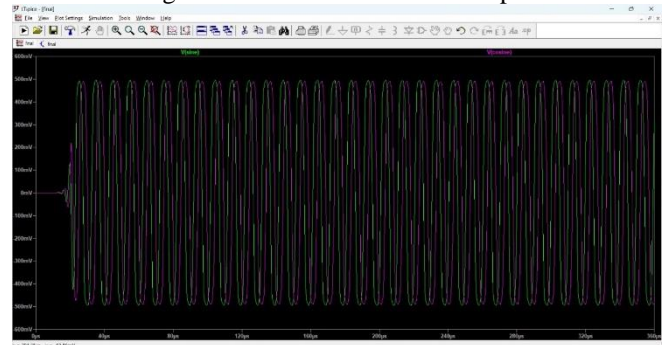


Fig.56: Transient simulation of oscillator output

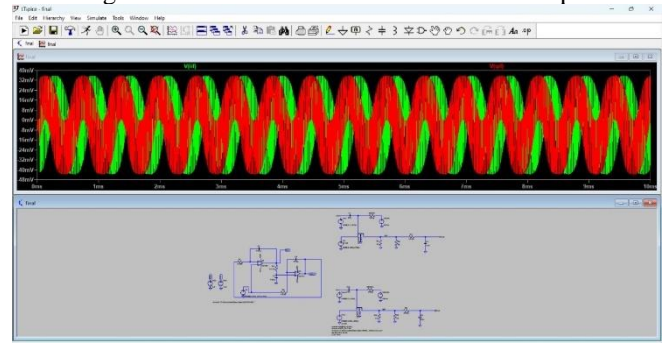


Fig.57: Transient simulation of IF and QF

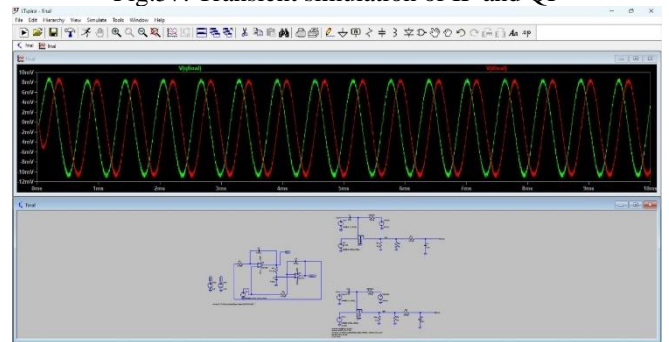


Fig.58: Transient simulation of IF(final) and QF(final)

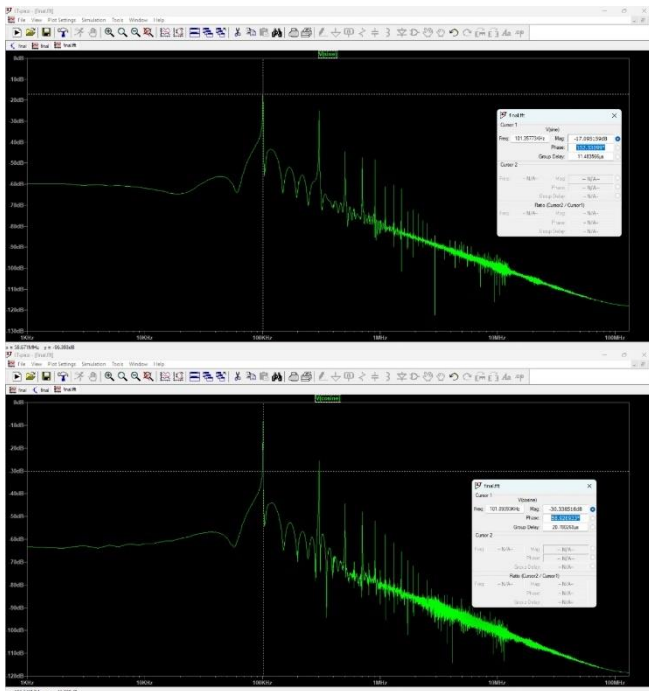


Fig.60: FFT plots of QF

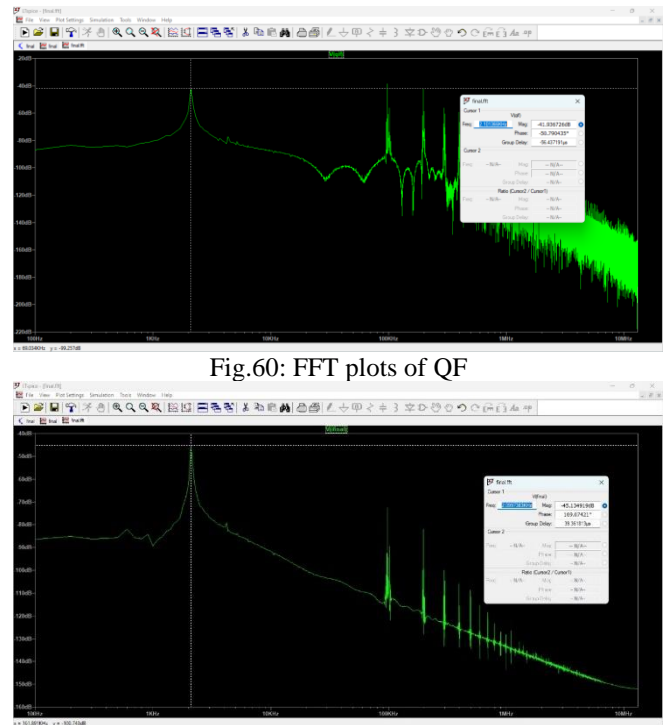


Fig.61: FFT plots of IF (final)

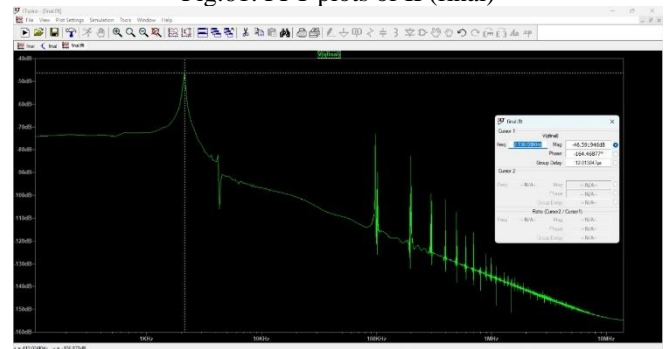


Fig.62: FFT plots of QF (final)

Yes. We can process the FFT plots to find the phase of final I and Q components.

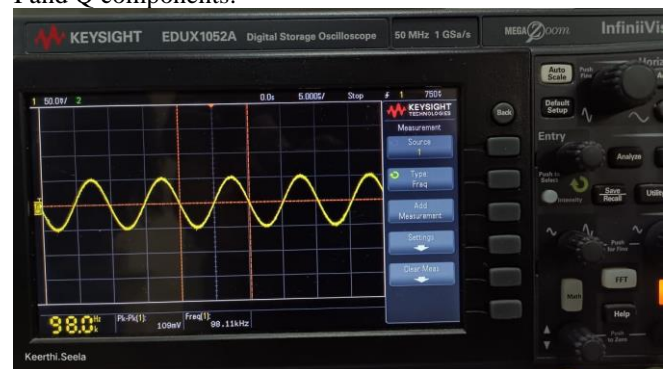


Fig.63: Transient plots of V_{IN}

To calculate phase diff

$$\phi_1 - \phi_2 = 2\pi f (t_{\text{peak sine}} - t_{\text{peak cosine}})$$

$$= 360 \times 100k \times (2.498 \mu s)$$

$(t_{\text{peak sine}} - t_{\text{peak cosine}})$ is obtained from transient simulations in Ltspice.

$$= 36 \times 2.498$$

$$= 89.928^\circ$$

$$\approx 90^\circ$$

The above three figures are reported to annotate the phase difference I-Q components

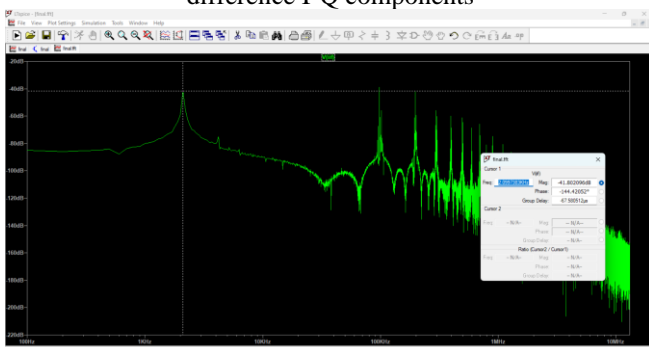


Fig.59: FFT plots of IF

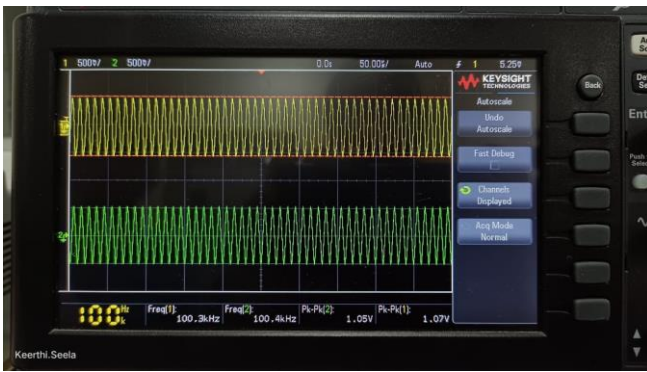


Fig.64: Transient plots of V_{OSCI} and V_{OSCQ}



Fig.68: Phase difference of V_{IFI} and V_{IFQ}

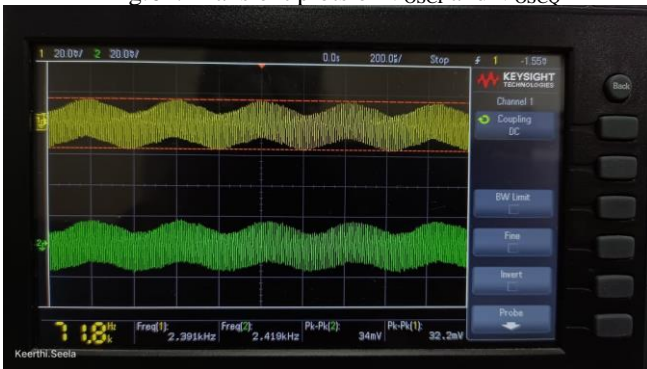


Fig.65: Transient plots of V_{IFI} and V_{IFQ}



Fig.69: Phase difference of $V_{IF(FINAL)I}$ and $V_{IF(FINAL)Q}$



Fig.66: Transient plots of $V_{IF(FINAL)I}$ and $V_{IF(FINAL)Q}$

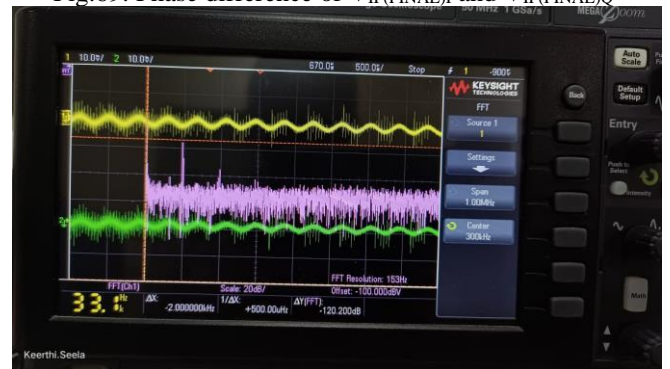


Fig.70: FFT plots of $V_{IF(FINAL)I}$

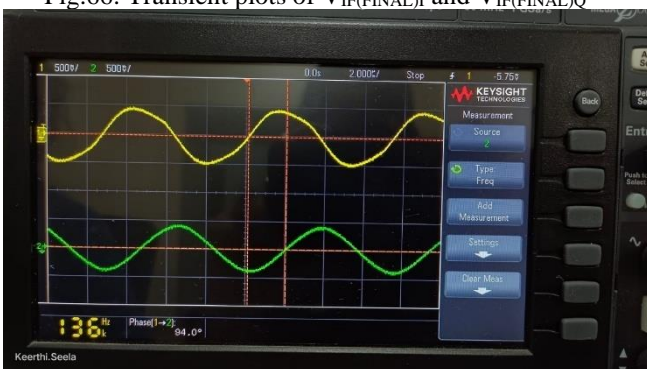


Fig.67: Phase difference of V_{OSCI} and V_{OSCQ}

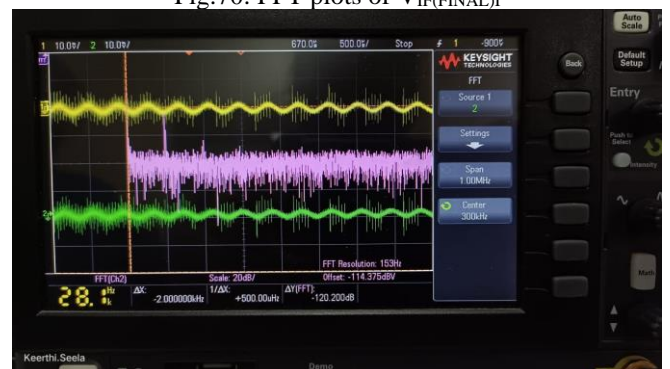


Fig.71: FFT plots of $V_{IF(FINAL)Q}$

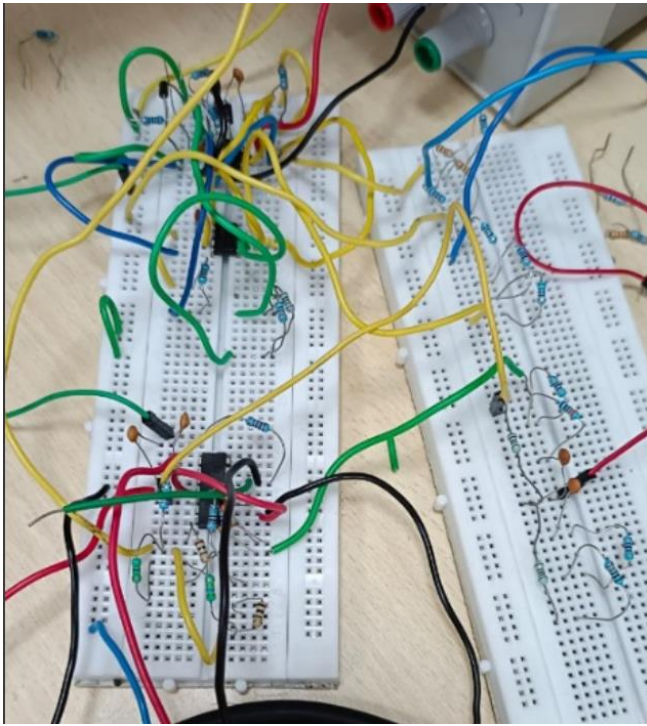


Fig.72: Circuit Overview

Parameters	Simulated	Measured
Oscillator Frequency (I-phase)	100kHz	100.3kHz
Oscillator Frequency (Q-phase)	100.18kHz	100.4kHz
Oscillator Amplitude (I-phase)	1V	1.05V
Oscillator Amplitude (Q-phase)	1V	1.07V
Input frequency	98kHz	98kHz
Supply – V_{DD}	2.5V	6.72V
Supply - V_{SS}	-2.5V	-6.72V
V_{BIAS}	0.5V	1.76V
C_C	27pF	5pF
R – LPF	7.9k Ω	8k Ω
C – LPF	10nF	10nF

VII. CONTRIBUTIONS

Keerthi Seela

- Simulations in LTSPICE
- Oscillator
- Report

Anumula Venkata Sai Sree Sahithi

- Mixer Circuit
- LPF
- Report and PPT